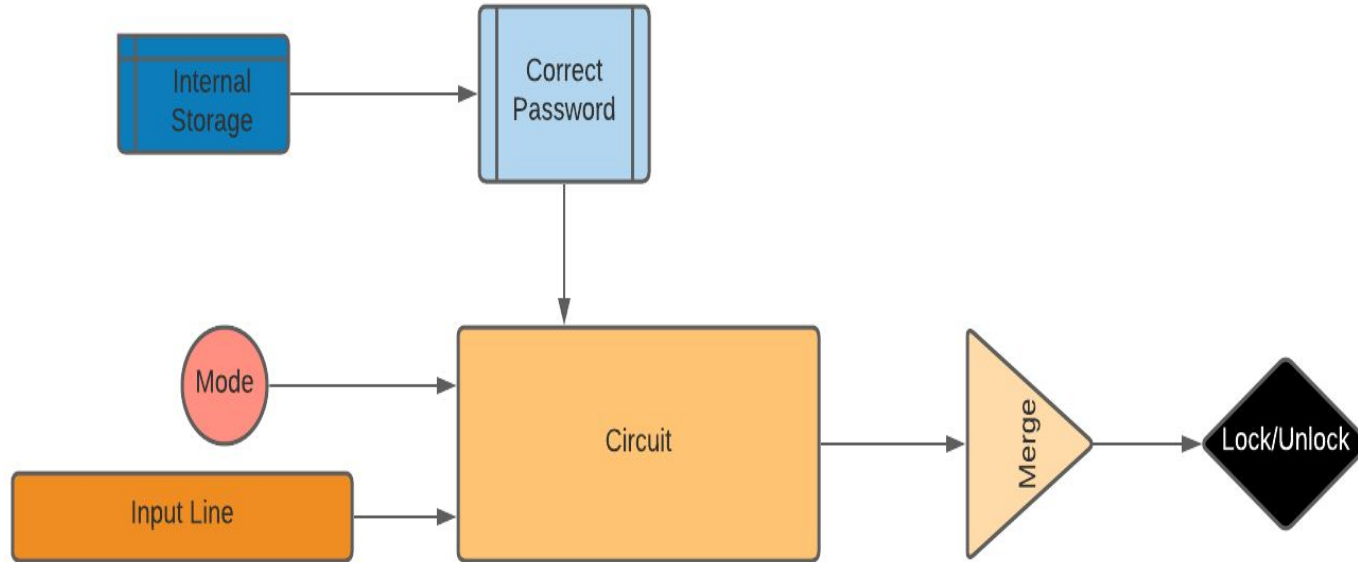




Digital Locking System

Design Assignment (Group = 80, Problem no. = 2)

Top Level Block Diagram




Working Logic


Main logic used in circuit is that XOR gate is used to detect different bits.

Output 1 means **LOCK**

Output 0 means **UNLOCK**

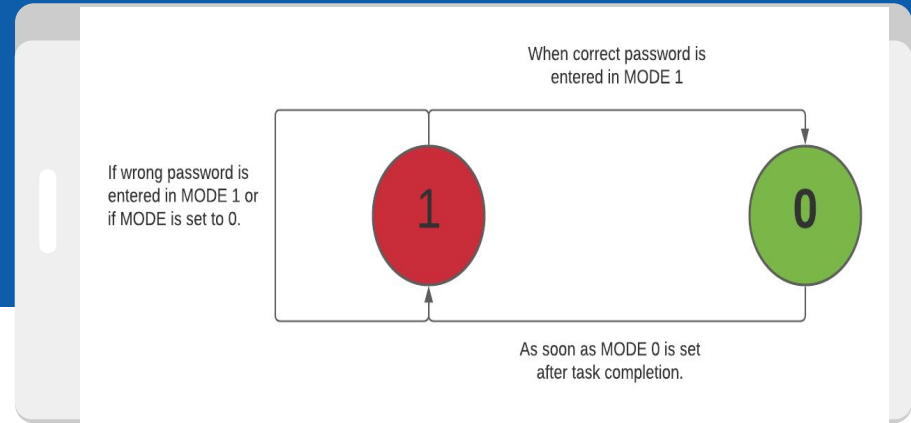Outputs are explained in figure attached.




 

Sample input and output

User input

Password: 9#\$1

 

If correct: 0

If incorrect: 1

Additional Functionalities

- BCD + ASCII characters input.
- Mode:
 - ◆ 0: Asynchronous Disable
 - ◆ 1: Operation Mode
- Automatic disable of unlock system as soon as wrong bit arrives.
- Automatic disconnect from clock input as soon as unlock till next sensory input.



- Connections done for separate memory for password reset, keep our circuit memory separate.

Thank you!

